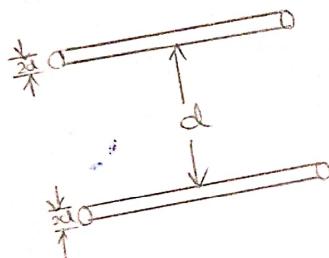


1. Explain different types of transmission line with neat sketches.


Types:

1. Parallel wireline (or) open wireline
2. Parallel plate (or) planar transmission line
3. Twisted wire
4. Wire above conducting plane
5. co-axial cable
6. wave guide
7. optical fibre
8. microstrip line
9. strip line

1. Parallel wireline (or) open wireline:-



Two wire parallel line

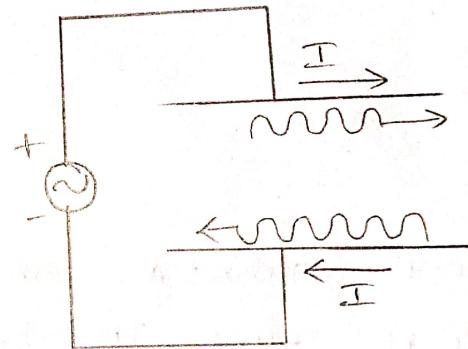

Potential difference

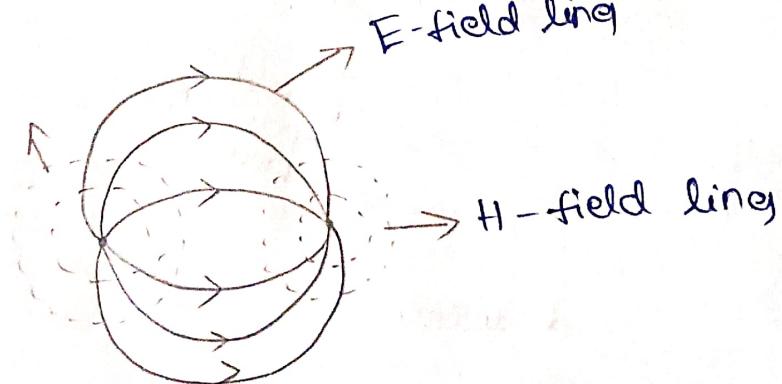


fig: Field lines [E&H]

- ⇒ Most commonly used transmission line.
- ⇒ Two parallel wires are separated by uniform distance $2a$ (or) a .
- ⇒ The current flows from one transmission wire to another transmission line.
- ⇒ Electric field and magnetic field are perpendicular to each other.


Advantages:

1. Simple structure.
2. Easy to construct.
3. Low cost.

Disadvantages:

1. As it is open transmission line structure it is capable of getting EM interference.
2. Above 100MHz there will be more Radiation loss.




2. Twisted pair of transmission line:-

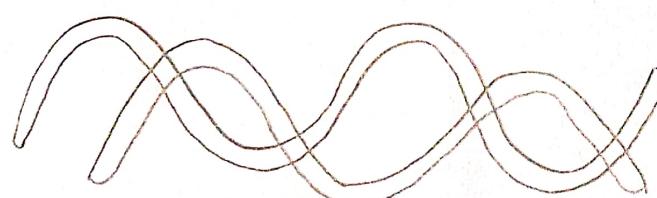

Two or more conductors are used.




Two or more wires are twisted and protected by insulator.

3. Parallel plate transmission line:

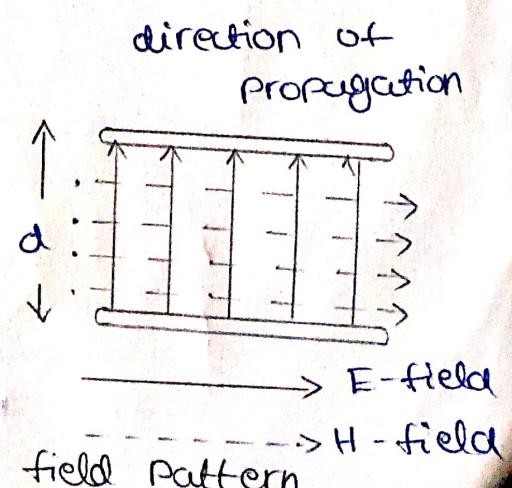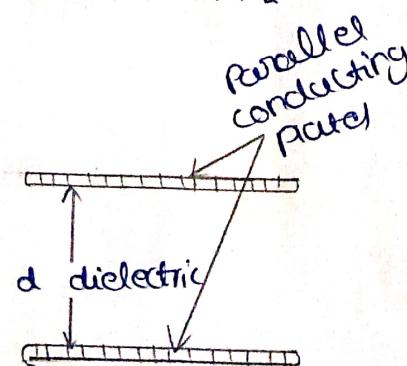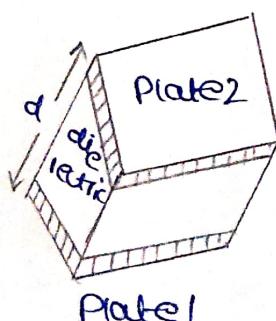

- ⇒ This transmission is used in PCB technology.
- ⇒ These plates are used for the closing of transmission antennae.

4. Coxial cable:

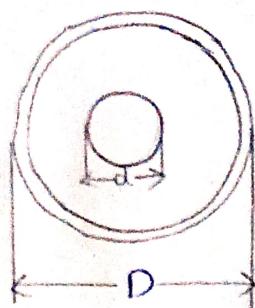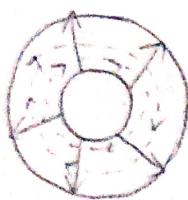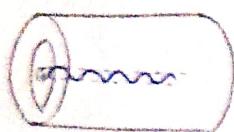

- ⇒ In this two conductors are used.

- ⇒ Signal is transmitted in hollow space.

Advantage:

1. Radiation losses are less they replace parallel plates.


Disadvantage:

1. Beyond 1GHz this becomes unstable.

Applications:

TV cables

5. Wave guides:

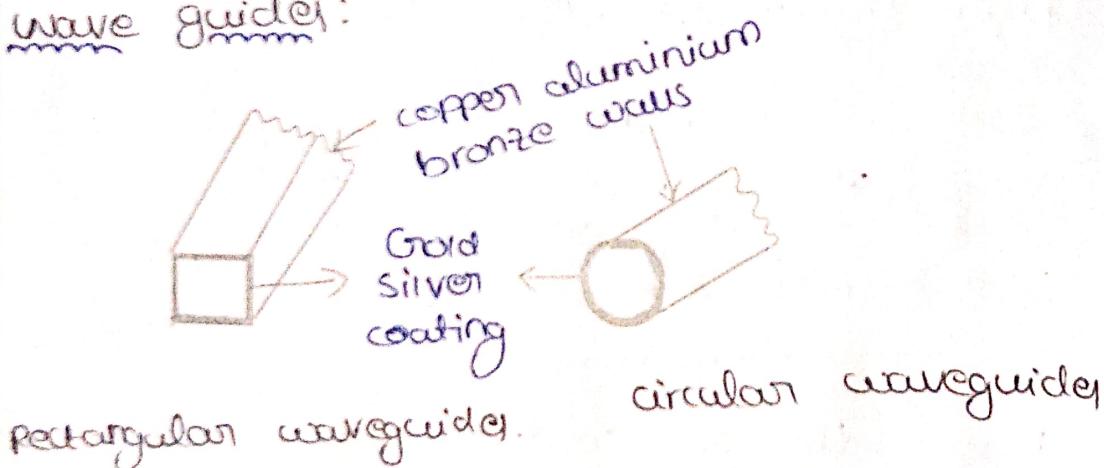

- ⇒ The wave guides are used in microwave frequencies.
- ⇒ Frequency is 300MHz to 300GHz.
- ⇒ Modes of propagation are TE, TM because of two conductors.

Advantages:

1. Power loss during propagation is negligible.

2. Large power handling capable.

3. As it is simple structure installation is easy.


Disadvantages:

1. Installation cost is high.

2. Not flexible.

3. Large in size.

6. optical fibre:

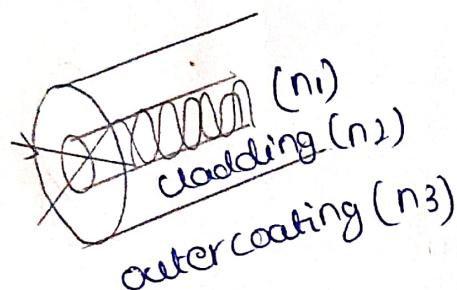

⇒ In this information in the form of light is travelled through it.

⇒ $n_1 > n_2$


Advantages:

1. Very high band width.

2. More efficiency

3. Small size.

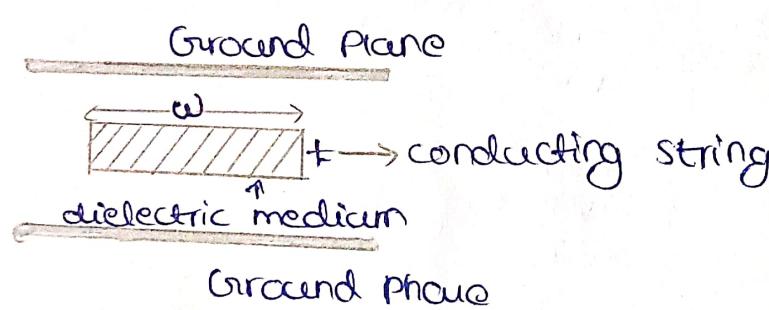7. strip line: (planar transmission line)



⇒ The signal travel through conducting strip.


⇒ The frequency range 100 MHz to 100 GHz.

⇒ In this we cannot tune the frequency range it is overcome in microstrip line.


⇒ The Ground plane and Ground plane are separated by dielectric medium.

2. Draw the equivalent circuit for an open wire transmission line and define primary constants of transmission line?

Equivalent circuit of Transmission line:

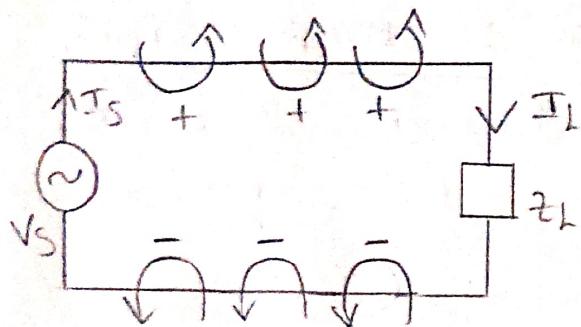

Transmission line with load

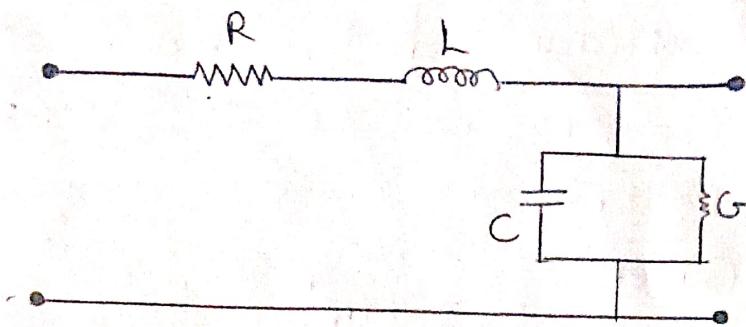

Equivalent circuit of two wire transmission line.

Primary constants of transmission line:

1. Resistance: When current is flowing through the conductor it must have resistance uniformly distributed all along the length of conductor.

$$R = \frac{\rho l}{a} \text{ ohms/km}$$

ρ = Resistivity

l = length of conductor

a = Radius of wire

2. Inductance:

The induced EMF in the transmission line resist the flow of current measured as inductance of wire.

$$L = \frac{N\phi}{I} \text{ H/km}$$

N = no. of turns of coil.

ϕ = magnetic field.

I = current.

3. Capacitance:

capacitance per unit length is given by

$$C = \frac{\epsilon A}{d} \text{ f/km}$$

ϵ = dielectric constant

A = area of cross section

d = distance between conductors.

4. Conductance:

It is measured as shunt conductance per unit length

units = Mhos/km.

3. A transmission line has $R=3\Omega/m$, $L=1\mu H/m$, $C=1\text{PF}/m$ and $G=0$ operated at $f=500\text{MHz}$. Find the attenuation constant of line.

Given,

$$R=3\Omega/m$$

$$L=1\mu H/m = 1 \times 10^{-8}$$

$$C=1\text{PF}/m = 1 \times 10^{12}$$

$$G=0$$

$$f=500\text{MHz}, \omega=2\pi f$$

$$= 2\pi \times 500 \times 10^6$$

$$= 1000\pi \times 10^6 = 10^9 \pi \text{ rad/s}$$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$\gamma = \sqrt{(3+j\pi \times 10^9 \times 10^{-8})(0+j\pi \times 10^9 \times 10^{12})}$$

$$\gamma = \sqrt{(3+j\pi \times 10^3)(j\pi \times 10^{-3})}$$

$$\gamma = \sqrt{(3+j3141.6)(j0.0031416)}$$

$$\gamma = \sqrt{-9.87 + j0.0094}$$


$$\gamma = 0.07 + j3.14$$

Attenuation constant $\alpha = 0.07 \text{ NP/m}$

Phase constant $\beta = 3.14 \text{ (or) } \pi \text{ rad/m}$

4. Derive T-Equivalent circuit of a transmission line?

T-Equivalent circuit:

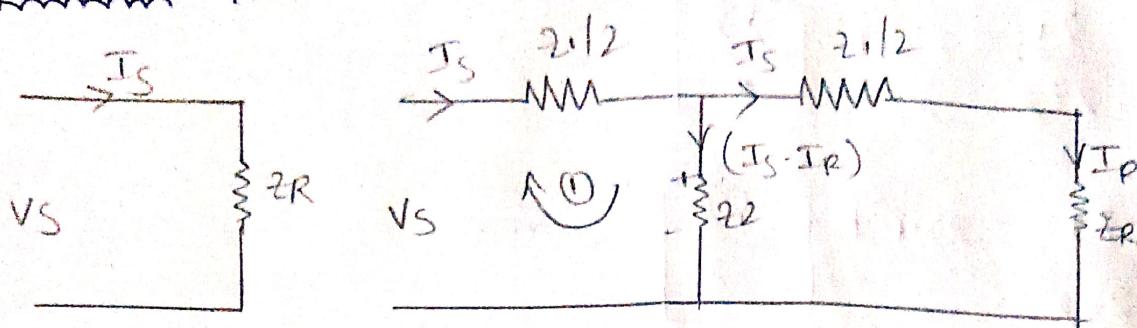

$$V_S = \frac{I_S Z_1}{2} - I_S (I_S - I_R) Z_2 = 0$$

$$V_S = \frac{I_S Z_1}{2} + I_S (I_S - I_R) Z_2$$

$$V_S = \frac{I_S Z_1}{2} + I_S Z_2 - I_R Z_2$$

$$I_R Z_2 = \frac{I_S Z_1}{2} + I_S Z_2 - V_S$$

$$I_R = \frac{I_S Z_1}{2 Z_2} + I_S - \frac{V_S}{Z_2}$$

$$I_R = I_S \left[1 + \frac{Z_1}{2 Z_2} \right] - \frac{V_S}{Z_2} \rightarrow ①$$

At $x=l$ current equation,

$$I_R = I_S \cosh \beta l - \frac{V_S}{Z_0} \sinh \beta l \rightarrow ②$$

compare Eq ① & ②

$$\cosh \beta l = 1 + \frac{Z_1}{2 Z_2} \rightarrow ③$$

$$\frac{\sinh \beta l}{Z_0} = \frac{1}{Z_2}$$

$$Z_2 = \frac{Z_0}{\sinh \beta l}$$

$$\rightarrow ④$$

from Eq ③

$$\frac{Z_1}{2 Z_2} = \cosh \beta l - 1$$

$$= 1 + 2 \sin^2 h \left(\frac{\rho l}{2} \right) - 1$$

$$\frac{z_1}{2z_2} = 2 \sinh^2 \left[\frac{\rho l}{2} \right]$$

$$\frac{z_1}{2z_2} = 2 \sin^2 h \left[\frac{\rho l}{2} \right]$$

$$\begin{aligned} \frac{z_1}{2} &= 2 \sin^2 h \left[\frac{\rho l}{2} \right] \cdot z_2 \\ &= 2 \sin^2 h \left(\frac{\rho l}{2} \right) \cdot z_2 \end{aligned}$$

$$= 2 \sinh \left(\frac{\rho l}{2} \right) \left(\frac{z_0}{\sinh \rho l} \right)$$

$$\frac{z_1}{2} = \frac{2 \sin^2 h \left(\frac{\rho l}{2} \right) z_0}{\sinh \rho l}$$

$$\frac{z_1}{2} = \frac{2 \sin^2 h \left(\frac{\rho l}{2} \right) z_0}{\sinh \rho l}$$

$$\frac{z_1}{2} = \frac{2 \sin^2 h \left(\frac{\rho l}{2} \right) z_0}{2 \sinh \left(\frac{\rho l}{2} \right) \cosh \left(\frac{\rho l}{2} \right)}$$

$$\frac{z_1}{2} = z_0 \cdot \tanh \left(\frac{\rho l}{2} \right)$$

5. Define and explain both loss less and distortion less line in terms of transmission line parameters.

loss less transmission line:

$$R = G = 0$$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

Real part:

$$d = \sqrt{LC} \left[\frac{R}{L} \right] = \sqrt{L} \cdot \sqrt{C} \left[\frac{R}{L} \right] \cdot \sqrt{L}$$

$$d = R \sqrt{\frac{C}{L}}$$

$$\beta = \omega \sqrt{LC}$$

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}} = \sqrt{\frac{L(R/L+j\omega)}{C(\omega/C+j\omega)}}$$
$$= \sqrt{\frac{L}{C}} \sqrt{\frac{R/L+j\omega}{R/L+j\omega}}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

phase velocity $v_p = \omega/\beta = \frac{\omega}{\omega \sqrt{LC}}$

$$v_p = \frac{1}{\sqrt{LC}}$$

6. Define wavelength, phase velocity and Group velocity. Derive the relation between Group velocity & phase velocity.

wavelength:

It is the distance that wave length travels along the line to have phase of 2π Radians.

$$\beta \delta = 2\pi$$

$$\delta = \frac{2\pi}{\beta} \text{ meters}$$

2. Phase velocity:

The velocity with which a wave of constant phase is propagating in transmission line is called phase velocity.

$$v_p = \omega/\beta \text{ km/sec}$$

$$= \sqrt{(j\omega L)(j\omega C)}$$

$$\alpha + j\beta = j\omega \sqrt{LC}$$

$$\alpha = 0; \beta = \omega \sqrt{LC}$$

$$Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

$$= \sqrt{\frac{j\omega L}{j\omega C}}$$

$$Z_0 = \sqrt{\frac{L}{C}}$$

$$\text{Phase velocity: } V_p = \frac{\omega}{\beta}$$

$$= \frac{\omega}{\omega \sqrt{LC}}$$

$$V_p = \frac{1}{\sqrt{LC}}$$

$$\text{since } V_p = \frac{1}{\sqrt{\mu E}}$$

$$\sqrt{\mu E} = \sqrt{LC}$$

Distortionless transmission:

$$\frac{R}{L} = \frac{G}{C}$$

$$\gamma = \sqrt{(R+j\omega L)(G+j\omega C)}$$

$$= \sqrt{L \left(\frac{R}{L} + j\omega \right) C \left(\frac{G}{C} + j\omega \right)}$$

$$= \sqrt{LC} \sqrt{\left(\frac{R}{L} + j\omega \right) \left(\frac{G}{C} + j\omega \right)}$$

$$\gamma = \sqrt{LC} \sqrt{\left(\frac{R}{L} + j\omega \right) \left(\frac{G}{C} + j\omega \right)}$$

$$= \sqrt{LC} \sqrt{\left(\frac{R}{L} + j\omega \right) \left(\frac{R}{L} + j\omega \right)}$$

$$\gamma = \sqrt{LC} \left(R/L + j\omega \right)$$

$$\gamma = \alpha + j\beta = \sqrt{LC} \left(\frac{R}{L} \right) + j\sqrt{LC} \cdot \omega$$

Group Velocity:

It is defined as the ratio of angular frequency to the changing phase constant.

$$V_g = \frac{\omega_2 - \omega_1}{\beta_2 - \beta_1} = \frac{d\omega}{dp} \text{ m/s}$$

Relation between Group Velocity & Group Velocity:

$$V_p = \frac{\omega}{\beta}$$

Differentiate both sides w.r.t ω ,

$$\frac{dV_p}{d\omega} = \beta \cdot \frac{d\omega}{d\omega} - \omega \cdot \frac{d\beta}{d\omega}$$

$$= \beta \left[1 - \frac{\omega}{\beta} \cdot \frac{d\beta}{d\omega} \right]$$

$$= \beta \left[1 - \frac{\omega}{\beta} \cdot \frac{dB}{d\omega} \right]$$

$$\frac{dV_p}{d\omega} = 1 - V_p \cdot \frac{dB}{d\omega}$$

$$\beta \cdot \frac{dV_p}{d\omega} = 1 - V_p \left[\frac{1}{V_g} \right]$$

$$\frac{V_p}{V_g} = 1 - \beta \cdot \frac{dV_p}{d\omega}$$

$$V_g = \frac{V_p}{1 - \beta \left(\frac{dV_p}{d\omega} \right)}$$

$$V_g = \frac{V_p}{1 - \omega \left[\frac{dV_p}{d\omega} \right]}$$